

EDLC

QP Code : 28703

(3 Hours)

[Total Marks : 100

- N.B. : (1) Question No.1 is Compulsory.
(2) Attempt any four out of remaining questions.

1. (a) Compare BJT and JFET 5
(b) Sketch the transfer characteristic curve for P channel JFET with $I_{DSS} = 5\text{mA}$, $V_p = 4\text{V}$. 5
(c) Draw and explain the block diagram of OPAMP. 5
(d) List characteristic features of 555 timer. 5
2. (a) Explain the Graphical determination of the h-parameters using characteristics curves of common emitter amplifier. 10
(b) Derive the Q point values (V_{DQ} & I_{DQ}) and current gain A_i for voltage divider Network for CE configuration. 10
3. (a) Derive equations of Z_i , Z_o , A_v for common source configuration using voltage divider network (with unbypassed R_s .) 10
(b) Explain the construction and working of JFET with its characteristic curves. 10
4. (a) Explain how an Op Amp can be used as: 10
(i) Integrator
(ii) Differentiator
(iii) Summing Amplifier.
(b) Using practical Op Amp realize the following relation - 10
 $V_0 = 5V_1 + 3V_2 - 5V_3$
5. (a) Explain CMRR and PSRR and an OPamp. 5
(b) Explain OP Amp as a ZCD. 5
(c) Explain instrumentation Amplifier using 3OP - AMPS and Derive the expression for voltage gain. 10
6. (a) Explain IC 555 timer as a monostable multivibrator with neat waveforms 10
(b) Design a +9V regulator using LM723 for current limit of 100mA. 10
7. Write short notes on (any two): 20
(a) PLL
(b) Inverting schmitt trigger
(c) D/A converter using R 2P resistor.

GE-Con. 10521-16.