

N.B. : (1) Question No.1 is compulsory

a2zSubjects.com


(2) Solve any three questions from remaining questions.

(3) Assume suitable data if it is required.

1. Solve any Four questions :

(a) Draw output waveform for following circuits.

5

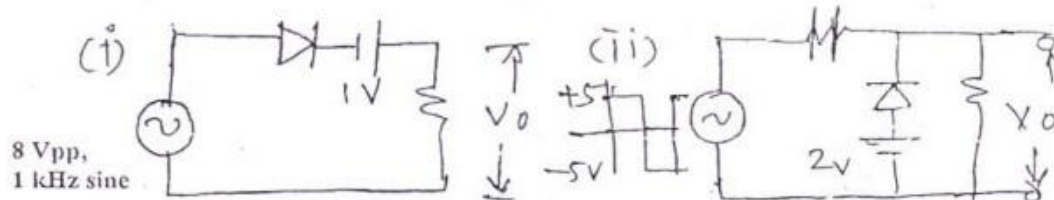

(b) Explain Wilson current source.

5

(c) What are different biasing methods used for FET, explain self bias technique.

5

(d) State and Explain Barkhausen criteria.


5

(e) Derive expression for efficiency for Class A transformer coupled amplifier.

5

2. (a) Find I_{CQ} , V_{CEQ} , R_i and R_o for following circuit with $R_C = 1.2 \text{ k}\Omega$.

10

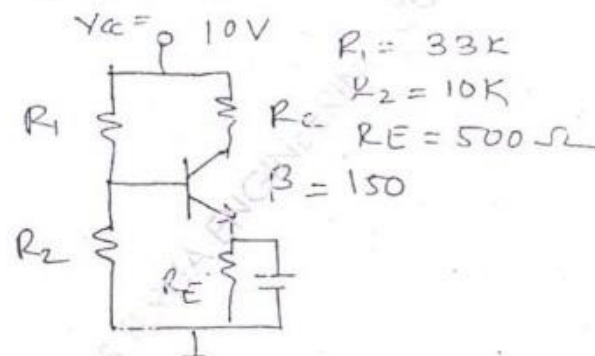


(b) Explain any one method for biasing for E-MOSFET.

10

3. (a) Find A_v , R_i and R_o for following circuit.


a2zSubjects.com

10

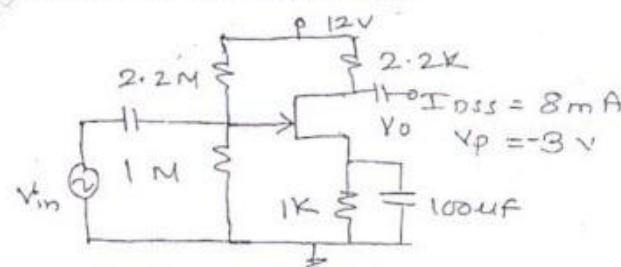

TURN OVER

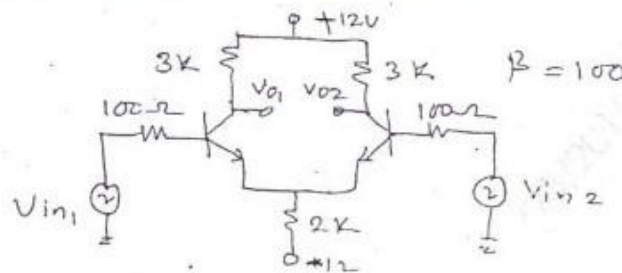- (b) Explain need for cascading of amplifiers. Explain CS-CE combination in detail. 10
4. (a) What is use of negative feedback in amplifier? Draw block diagram for current shunt feedback and find A_f , R_{if} and R_{of} . 10
- (b) Explain High frequency response of CS-CS amplifier and hence derive equation of output frequency. 10
5. (a) For the following diff-amp find A_d , A_c and CMRR. 10



- (b) Explain working of Class B push-pull power amplifier. What is cross over distortion? 10
6. Write short notes on (any four) 20
- High frequency oscillator,
 - Cascode amplifier,
 - High frequency model for BJT
 - Heat sinks
 - Constant current source used in diff-amp.