

INST CBES

REI/VI/INST/Signal Conditioning Ckt
(3 Hours)

Q.P. Code : 5653

Design / 01.12.15

[Total Marks : 80]

1. Question no. 1 is compulsory
2. Attempt any three questions from remaining five questions.
3. Figures to the right indicate full marks
4. Assume suitable data whenever necessary

Duration : 03 hours

Marks : 80

- | | | |
|------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| Q.1. | a. With a suitable diagram discuss the concept of loading and how to avoid it. | 20 |
| | b. Draw the circuit of practical Integrator and its output waveforms. | |
| | c. Draw the circuit of Zero crossing detector and its output waveforms. | |
| | d. Explain the significance of all-pass filters. muADDA.com | |
| Q.2. | a. Explain successive approximation analog to digital converter with diagram. | 10 |
| | b. Draw and explain circuit diagram of absolute value circuit using op-amp. Discuss its advantages over traditional diode rectifier. | 10 |
| Q.3. | a. Draw and explain the operation of Temperature compensated Log amplifier. | 10 |
| | b. What are the advantages of active filters over passive filters. Design a second-order band pass filter for given $F_H=2\text{KHz}$, $F_L=300\text{Hz}$ and Pass band gain=4. | 10 |
| Q.4. | a. Design and Explain operation of Astable Multivibrator using IC555 for 60% duty cycle. | 10 |
| | b. A sensor outputs a range of 20.0 to 250mV as a variable varies over its range. Develop signal conditioning so that this becomes 0 to 5V. The circuit must have very high input impedance. | 10 |
| Q.5. | A RTD has $\alpha(T)=0.005/^\circ\text{C}$, $R=500\Omega$, and a dissipation constant of $PD=30\text{mW}/^\circ\text{C}$ at 20°C . The RTD is used in a bridge circuit with $R_1 = R_2 = 500\Omega$ and R_3 a variable resistor used to null the bridge. If the supply is 10 V and the RTD is placed in a bath at 0°C , find the value of R_3 to null the bridge. muADDA.com | 10 |
| | b. Draw and explain the principle and construction of thermocouple. What is the signal conditioning associated with it. | 10 |
| Q.6: | Write short notes on : (any four) | 20 |
| | a. Sample and hold circuit | |
| | b. Phase Locked loop | |
| | c. Variable voltage regulator | |
| | d. Data Acquisition System | |
| | e. Flash type ADC | |
| | f. SMPS | |