

SE Sem - IV (Biomed.)
Sem. IV (Biomed) CBGS

29/5/14

ECD - II
Electronic Circuit Analysis & Design - II
QP Code : NP-19767


(3 Hours)

20

[Total Marks : 80

- N.B. : (1) Question No. 1 is compulsory.
(2) Answer any three questions from remaining five questions.
(3) Assume suitable data if necessary.

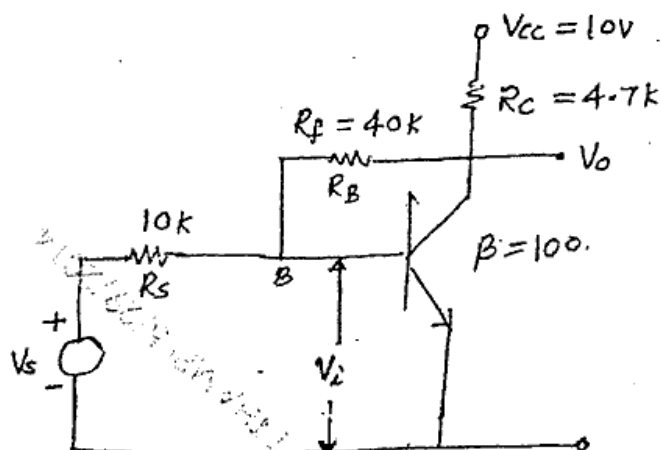1. (a) Explain any two electrical characteristics of op-amp. Give its ideal and practical values. 5
- (b) Explain the advantages and limitations of use of swamping resistor in differential amplifier. 5
- (c) Distinguish Class B and Class C power amplifier. 5
- (d) Explain zero crossing detector. 5
2. (a) Compare various types of negative feedback. (Block diagram compulsory). 10
- (b) For the circuit shown in figure identify the feedback topology. Using negative feedback approach, determine A_{vf} , R_{if} and R_{of} . 10



3. (a) Derive expressions for input resistance, output resistance and voltage gain, CMRR for single input balanced output differential amplifier. 10
 - (b) For the following given specifications for the dual input balanced output differential amplifier, 10
- $R_c = 2.2 K$, $R_1 = 4.7 K$, $R_{in1} = R_{in2} = 50 \Omega$,
 $R_E = 1 K$, $V_{CC} = 20 V$, $V_{EE} = -20 V$,
 $\beta_{dc} = \beta_{ac} = 100$, $V_{BE} = 0.7 V$.

Determine the quiescent collector current, collector to emitter voltage V_{CEQ} . Also calculate A_d , A_c , CMRR, R_{in} and R_o .

[TURN OVER.

Con. 12224-14.

Sem IV (Biomed) - CBGS

ECD - II

2

QP Code : NP-19767

4. (a) Derive expressions for maximum efficiency of transformer coupled class A amplifiers and also for class B amplifier. 10
- (b) Design class A transformer coupled amplifier to provide 12 W power to the speaker of 10 Ω . 10
5. (a) Derive a relation for frequency of oscillations and condition for sustained oscillations of Wein Bridge Oscillator. 10
- (b) Design following circuits using op-amp :- 10
- (i) A sine wave of 1 KHz frequency.
- (ii) $V_0 = - \int V_{in} \cdot dt$
6. Explain following applications of op-amp (any two) :- 20
- (a) Temperature compensated log amplifier.
- (b) Instrumentation amplifier.
- (c) Precision rectifier.

Con. 12224-14.

DBEC DATA SHEET

Transistor type	P _{dm} max @ 25°C Watts	I _{em} max @ 25°C Amps	V _{ce} (sat) volts d.c.	V _{ce} (sat) volts d.c.	V _{ce} (Sat) volts d.c.	V _{ce} (Sat) volts d.c.	V _{ce} (Sat) volts d.c.	D.C. current gain		Signal gain	h _{FE} max.	V _{BE} max.				
								min	max.				min.	typ.	max.	
2N3055	115-5	15-0	1-1	100	60	70	90	7	200	20	50	70	15	50	120	1-8
2N3055	50-0	5-0	1-0	60	50	55	60	5	200	25	50	100	25	75	125	1-5
2N3055	30-0	4-0	1-0	50	40	—	—	8	150	30	50	110	33	60	115	1-2
2N3055	5-0	0-7	0-6	70	60	65	—	6	200	50	90	280	50	90	280	0-9
2N3055	0-25	0-1	0-25	50	45	50	—	6	125	115	180	220	125	220	260	0-9
2N3055 (PNP)	0-225	0-5	0-25	85	30	—	—	—	100	35	—	65	—	45	—	—
2N3055	0-25	0-1	0-25	50	45	50	—	6	125	200	290	450	240	330	500	0-9

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	h _{ie}	h _{oe}	h _{re}	h _{fe}	-V _{GS} volts		I _{DS} mA		-V _{DS} Volts		r _d	Derate above 25°C				
					min.	max.	min.	max.	min.	max.						
BC 147A	2.7 K Ω	18 μ U	1.5 × 10 ⁻⁴	0.4°C/mw	0-0	0-2	0-4	0-6	0-11	1-0	1-2	1-6	2-0	2-4	2-5	3-0
2N 525 (PNP)	1.4 K Ω	25 μ U	3.2 × 10 ⁻⁴	—	1-0	9-0	8-3	7-6	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1
BC 147B	4.5 K Ω	30 μ U	2 × 10 ⁻⁴	0-4°C/mw	7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-8	0-2	0-0	0-0
BC 147B	—	—	—	—	4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0

N-Channel JFET

Type	V _{GS} max. Volts	V _{DS} max. Volts	P _d max. @ 25°C	T _J max.	I _{DS}	r _d	-V _{GS} Volts	r _d	Derate above 25°C
2N3822	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C
BFW 11 (typical)	30	30	300 mW	200°C	7 mA	5000 μΩ	2.5	50 KΩ	—

JIT type	P _d max. @ 25°C	I _p max.	V _{GS} max.	V _{DS} max.	T _J max.	η	R _{th} KΩ	I _p max.
2N7645	300mW	50mA	2Amp.	30	125°C	0.50	4.7	9-1