

N.B. : (1) Question no. 1 is compulsory.

(2) Solve any **three** questions out of remaining **five** questions.

(3) **Figures** to the **right** indicate **full** marks.

(4) Solve **one complete** question together.

a2zSubjects.com

(5) **Assume** suitable **data** wherever **necessary**.

1. Attempt any **four** from the following:-

(a) What are the advantages of SVM over the conventional Sine wave PWM? Explain. 5

(b) List the merits and demerits of online and offline UPS. 5

(c) Explain regenerative braking for DC motors. 5

(d) Explain in brief the effect of source inductance in single phase fully controlled bridge rectifier. 5


(e) Explain the concept of UPS and give classification of UPS system. 5

2. (a) Explain clearly the steps involved in Space Vector Modulation for three phase voltage source inverter. 10

(b) A single phase full-wave mid-point converter with freewheeling diode as shown below in Fig. Q2(b) is supplied from a 120V, 50 Hz supply with a source inductance of 0.33 mHenry. Assuming that the load current is continuous at 4A, find the overlap angle for

(i) Transfer of current from a conducting thyristor to the commutating diode.

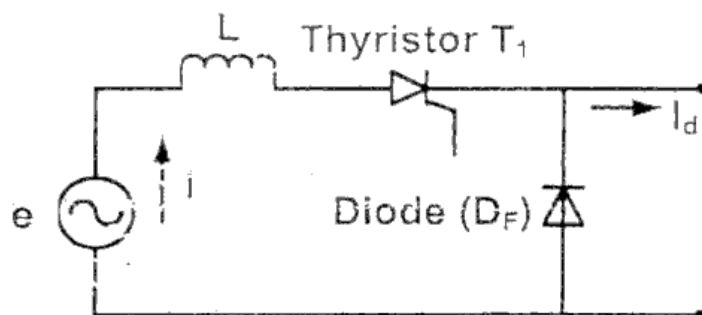(ii) From the commutating diode to a thyristor when the firing angle is 15 degree.



a2zSubjects.com

Fig.Q2 (b)

3. (a) Derive and explain the state-space model of Buck converter. 10

(b) Explain the PI (Proportional + Integral) control of DC-DC converter with the help of neat diagram. 10

a2zSubjects.com

4. (a) Derive the expressions for output voltage and current for a single phase fully controlled bridge rectifier with source inductance using equivalent circuit. 8

(b) What are SMPS? Give classification and explain any SMPS circuit in detail. 6

(c) Draw and explain the battery charging circuit involving power electronics system. 6

[TURN OVER

5. (a) A separately excited DC motor is supplied from 230V, 50Hz source through a single-phase half wave controlled converter. Its field is fed through single-phase semi-converter with zero degree firing angle delay. 10
Motor resistance = 0.70Ω , Motor constant = 0.5 volts sec/rad.
For a rated load torque of 15 NM at 1000 rpm and for continuous ripple-free current, determine:
- (i) Firing angle delay of the armature converter.
 - (ii) RMS value of thyristor & freewheeling diode current.
 - (iii) Input power factor of the armature current.
- (b) Explain various methods of speed control for 3-phase induction motor. 10
6. Write short notes on:
- (a) Comparison of fly-back and forward converters used in SMPS. 7
 - (b) Power electronics applications in induction heating. 6
 - (c) Slip power recovery scheme for induction motor using Kramer Drive below sub-synchronous speed. 7
-