

S.E. (SEM. IV) (CBSGS) (MECHANICAL ENGG.)
INDUSTRIAL ELECTRONICS

10th June 2016
3.00 pm to 6.00 pm

Mechanical/Automobile

QP Code : 555701

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 is compulsory.
(2) Attempt any three questions out of remaining questions.
(3) Figures to the right indicate full marks.
(4) Assume suitable data if necessary.

- | | |
|--|----|
| 1. Solve any four :- | 20 |
| (a) Enlist four applications of SCR-diode circuit. | |
| (b) What is the basic principle of bridge configured converter circuit? | |
| (c) Explain the operation of voltage follower circuit. | |
| (d) Define and describe logic operation, power dissipation and propagation delay in digital circuits. | |
| (e) What is a brushless dc motor? Give its two applications. | |
| 2 (a) What is GTO? Explain its working. What are similarities between GTO and SCR? | 7 |
| (b) State and describe power MOSFET on the basis of construction, principles of operation, applications, rating, input and output characteristics. | 7 |
| (c) Derive the output voltage for full wave fully controlled rectifier and find the firing angle for maximum output. | 6 |
| 3 (a) Explain in detail the concept of R-L-E load in converters. | 7 |
| (b) Classify speed control of ac motor and describe any one using block diagram. | 7 |
| (c) How does driver circuit work? Illustrate with an example. | 6 |
| 4 (a) Explain in detail first order low pass active filter. | 7 |
| (b) What is difference between combinational and differential circuits? | 7 |
| (c) Discuss speed torque characteristics of dc motor? Classify types of loads on the basis of time duration. | 6 |
| 5 (a) Describe the functional block diagram and architecture of MSP430 microcontroller? | 7 |
| (b) Realize basic digital gates using NOR and NAND universal gates. | 7 |
| (c) Write a program using MSP430 for external input and output devices. | 6 |
| 6 (a) Select a motor for machine tools application and describe with the speed torque characteristics. | 7 |
| (b) Compare microprocessor and microcontroller. | 6 |
| (c) Explain minimum six distinguishing features of MSP430 microcontroller. | |